

Title: Basic Electrical Engineering

Author: D.P. Kothari

Edition: 5th Edition

Chapter 1: DC Circuits

Ohm's law states that $V = I R$, relating voltage V , current I and resistance R in a linear resistive element.

Example 1.1: A resistor of 10 ohm carries a current of 2 A. Find the voltage drop V across it and the power P dissipated.